

Circuits Problem Set

Akhil Waghmare

April 10, 2015

1 Equations Review

Ohm's Law - $V = IR$

Capacitance - $C = \frac{Q}{V}$


Capacitance for Parallel Plate Capacitor - $C = \frac{\epsilon_0 A}{d}$

Energy in Capacitor - $U = \frac{1}{2}CV^2 = \frac{1}{2}QV = \frac{Q^2}{2C}$


Power Dissipation for Resistor - $P = IV = I^2R = \frac{V^2}{R}$

2 Problems

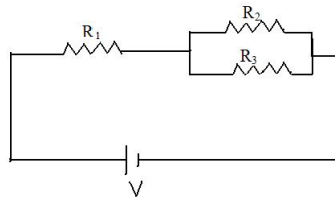- Below is a diagram of a circuit with resistors of resistance R_1 , R_2 , and R_3 , and it has a voltage source with potential V . For each resistor determine the voltage across it, the current through it, and the power dissipated by it.



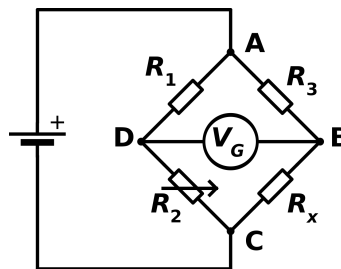- The circuit arrangement below is known as a *Wheatstone bridge*. It consists of a battery with a potential ϵ , two resistors with known resistance (R_1 and R_3), a variable resistor R_2 , and a resistor with unknown resistance R_x . If no current flows in the wire connecting points B and D , show that $R_1R_x = R_2R_3$.



- We can specifically control the capacitance of a specific capacitor by introducing a *dielectric* with dielectric constant κ , a material that is inserted into the empty space between the plates and increases its capacitance by a factor of κ . Say we are interested in inserting two dielectrics into a capacitor in the configurations shown below. Find the final capacitance of the capacitor in each scenario.

